

Simple Voltage Divider Calculator with *Uncertainty* Calculated via Partial Derivatives

Note
Variance is for an stats study.

Absolute Uncertainty of f

$$\Delta_{abs}(f\#) := \left[\begin{array}{c} x\# := \text{Unknowns}(f\#) \quad fs\# := \text{num2str}(f\#) \quad xs\# := \overline{\text{num2str}(x\#)} \\ f\# \\ \sum_{k\#=1}^{\text{length}(xs\#)} \text{str2num}\left(\text{concat}\left(\text{"abs(diff(", fs\#, ", ", xs\#_{k\#}, "))*\Delta", xs\#_{k\#}}\right)\right) \end{array} \right]$$

Relative Uncertainty of f

$$\Delta_{rel}(f\#) := \left[\begin{array}{c} x\# := \text{Unknowns}(f\#) \quad fs\# := \text{num2str}(f\#) \quad xs\# := \overline{\text{num2str}(x\#)} \\ f\# \\ \frac{1}{f\#} \cdot \sum_{k\#=1}^{\text{length}(xs\#)} \text{str2num}\left(\text{concat}\left(\text{"abs(diff(", fs\#, ", ", xs\#_{k\#}, "))*\Delta", xs\#_{k\#}}\right)\right) \cdot x\#_{k\#} \end{array} \right]$$

Inputs:

Input voltage

$$V_{in} := 27 \text{ V}$$

Upper voltage divider resistor R1

$$R1 := 20 \text{ k}\Omega$$

Lower voltage divider resistor R2

$$R2 := 30 \text{ k}\Omega$$

Input voltage variance

$$\Delta V_{in} := 1 \% \cdot V_{in}$$


R1 variance using tol

$$\Delta R1 := 2 \% \cdot R1$$

R2 variance using tol

$$\Delta R2 := 5 \% \cdot R2$$

Simple Voltage Divider

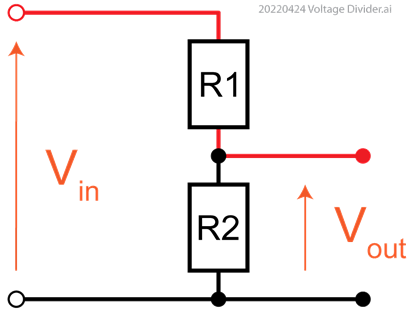

Formulas:

Vout formula

$$\Delta := \left[\begin{array}{c} \text{Clear}(V_{in}, R1, R2) \\ \Delta_{abs}\left(V_{in} \cdot \frac{R2}{R1 + R2}\right) \end{array} \right] \quad \left[\begin{array}{c} V_{out} \\ \Delta V_{out} \end{array} \right] := \Delta$$

Outputs:

Nominal output voltage

$$V_{out} = 16.2 \text{ V}$$

Output voltage variance

$$\Delta V_{out} = 615.6 \text{ mV}$$

Nominal output voltage range

$$V_{out} \pm \Delta V_{out} = \begin{cases} 16.8156 \\ 15.5844 \end{cases} \text{ V}$$

With relative uncertainties

$$\Delta V_{in} := 1 \%$$

$$\Delta R1 := 2 \%$$

$$\Delta R2 := 5 \%$$

Formulas:

Vout formula

$$\Delta := \left[\begin{array}{c} \text{Clear}(V_{in}, R1, R2) \\ \Delta_{rel}\left(V_{in} \cdot \frac{R2}{R1 + R2}\right) \end{array} \right] \quad \left[\begin{array}{c} V_{out} \\ \Delta V_{out} \end{array} \right] := \Delta$$

Outputs:

Nominal output voltage

$V_{out} = 16.2 \text{ V}$

Output voltage variance

$\Delta V_{out} = 3.8 \%$

Nominal output voltage range

$V_{out} \cdot (1 \pm \Delta V_{out}) = \begin{cases} 16.8156 \\ 15.5844 \end{cases} \text{ V}$

Alvaro