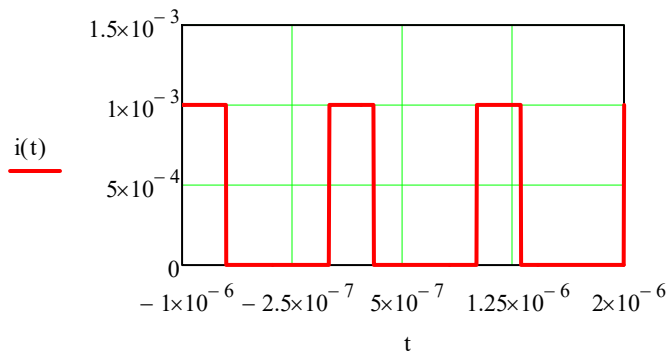


$$T_s := 10^{-6} \quad D := 0.3 \quad I_{\text{peak}} := 10^{-3}$$


$$(0 < D < 1)$$

$$i(t) := \begin{cases} \tau \leftarrow \text{mod}(t, T_s) \\ \tau \leftarrow \tau + T_s \text{ if } \tau < 0 \\ i \leftarrow I_{\text{peak}} \text{ if } 0 \leq \tau < DT_s \\ i \leftarrow 0 \text{ if } D \cdot T_s \leq \tau < T_s \\ i \end{cases}$$

mod(x, y) Returns the remainder on dividing x by y (x modulo y).
Result has the same sign as x.



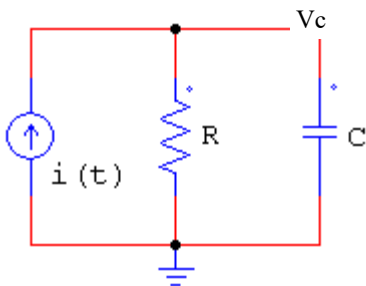The current $i(t)$ defined above is used as excitation source for the circuit



$$R1 := 1000$$

$$C1 := 10^{-8}$$

Define a voltage for the unknown node $V_c(t)$.
Current in the resistor can be calculated $i_R(t)$

$$i_{R1}(t) = \frac{V_c(t)}{R1}$$

Kirchoffs current law will give the charging current for the capacitor

$$i_{C1}(t) = i(t) - i_{R1}(t)$$

which then defines an ODE that mathcad can solve

$$\frac{d}{dt}V_c(t) = \frac{1}{C1} \cdot i_{c1}(t)$$

Note that mathcad struggles with units so may be easier to set up without them, but the final result is much easier to understand & modify with them
Also for presentation purposes it is 'neater'

$$t_{\text{end}} := 20 \cdot T_s$$

Given

$$\frac{d}{dt}V_c(t) = \frac{1}{C1} \cdot \left(i(t) - \frac{V_c(t)}{R1} \right)$$

$$V_c(0) = 0 \quad \text{Assume capacitor initial voltage is 0V}$$

$$V_c := \text{Odesolve}(t, t_{\text{end}})$$

